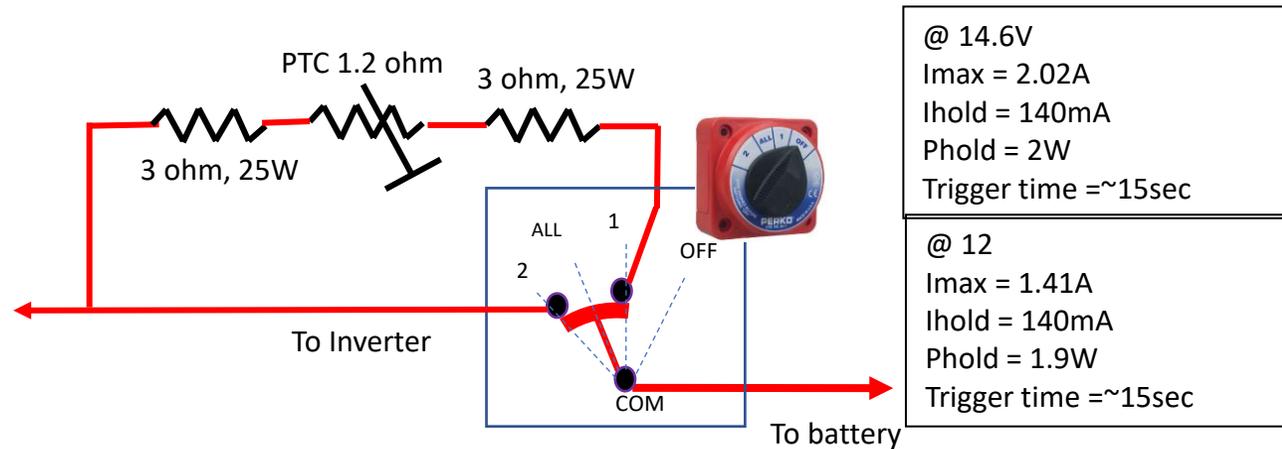


## **Inverter Disconnect with pre-charge**

This circuit is designed as an inverter disconnect that allows the user to pre-charge the inverter capacitors before fully turning on the system.

# 12V SYSTEM



@ 14.6V  
 $I_{max} = 2.02A$   
 $I_{hold} = 140mA$   
 $P_{hold} = 2W$   
 Trigger time  $\approx 15sec$

---

@ 12  
 $I_{max} = 1.41A$   
 $I_{hold} = 140mA$   
 $P_{hold} = 1.9W$   
 Trigger time  $\approx 15sec$

## Operation:

### Turn ON

1. Ensure inverter is off
2. Turn switch to position '1' for  $\sim 1$  second
3. Turn switch to position 'All' or '2'
4. Turn on inverter

## PTC specs


| Bulk Part Number   | Max. voltage | *1<br>Resistance Value at +25 °C | *2<br>Max. Current | *3<br>Hold Current |       | *4<br>Trip current |        | Dimensions (mm) |      |     |
|--------------------|--------------|----------------------------------|--------------------|--------------------|-------|--------------------|--------|-----------------|------|-----|
| Taping Part Number |              |                                  |                    | +105°C             | +85°C | -10°C              | -40°C  | D               | H    | d   |
| PTGLCSAS1R2K3B51B0 | D.C.<br>51V  | 1.2ohm $\pm$ 10%                 | 5.0A               | 315mA              | 449mA | 1168mA             | 1270mA | 11.5            | 16.5 | 0.6 |
| PTGLCSAS1R2K3B51A0 |              |                                  |                    |                    |       |                    |        |                 |      |     |

Note: The PTC resistor is a safety that covers a miss-use of the switch.

If the user leaves the inverter 'On' and the switch in position 1, there may be significant current going through the resistor and over-heating it. In this case, the PTC will heat up first and will significantly reduce the current after several seconds. If the switch is used properly, this should never happen and there will be almost no heat build-up.

An alternative to the PTC is use a single 50W 10 ohm resistor in place of the ptc and two resistors. However, in this case, you might need to mount the resistor on a heat sync external to the switch in order to dissipate the heat in a miss-use condition.

## 24V SYSTEM

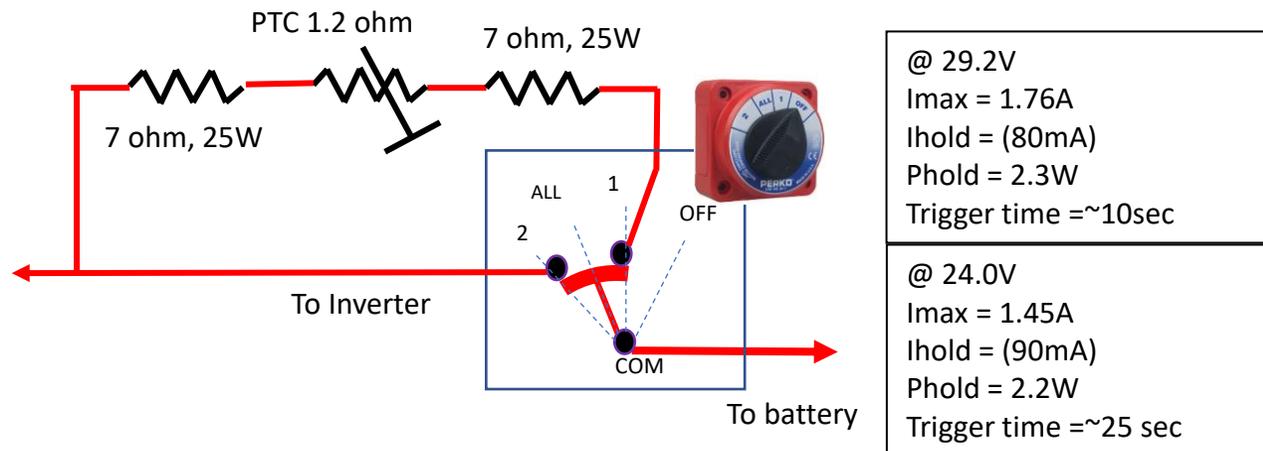

### Operation:

#### Turn ON

1. Ensure inverter is off
2. Turn switch to position '1' for  $\sim 1$  second
3. Turn switch to position 'All' or '2'
4. Turn on inverter

#### Turn Off

1. Turn off Inverter.
2. Turn Disconnect switch to 'Off' position.

### PTC specs

| Bulk Part Number   | Max. voltage | *1 Resistance Value at +25 °C | *2 Max. Current | *3 Hold Current |       | *4 Trip current |        | Dimensions (mm) |      |     |
|--------------------|--------------|-------------------------------|-----------------|-----------------|-------|-----------------|--------|-----------------|------|-----|
|                    |              |                               |                 | +105°C          | +85°C | -10°C           | -40°C  | D               | H    | d   |
| PTGLCSAS1R2K3B51B0 | D.C. 51V     | 1.2ohm $\pm$ 10%              | 5.0A            | 315mA           | 449mA | 1168mA          | 1270mA | 11.5            | 16.5 | 0.6 |
| PTGLCSAS1R2K3B51A0 |              |                               |                 |                 |       |                 |        |                 |      |     |


Note: The PTC resistor is a safety that covers a miss-use of the switch.

If the user leaves the inverter 'On' and the switch in position 1, there may be significant current going through the resistor and over-heating it. In this case, the PTC will heat up first and will significantly reduce the current after several seconds. If the switch is used properly, this should never happen and there will be almost no heat build-up.

An alternative to the PTC is use a single 50W 20 ohm resistor in place of the ptc and two resistors. However, in this case, you would need to mount the resistor on a heat sync external to the switch in order to dissipate the heat during a miss-use condition.

# 48V SYSTEM

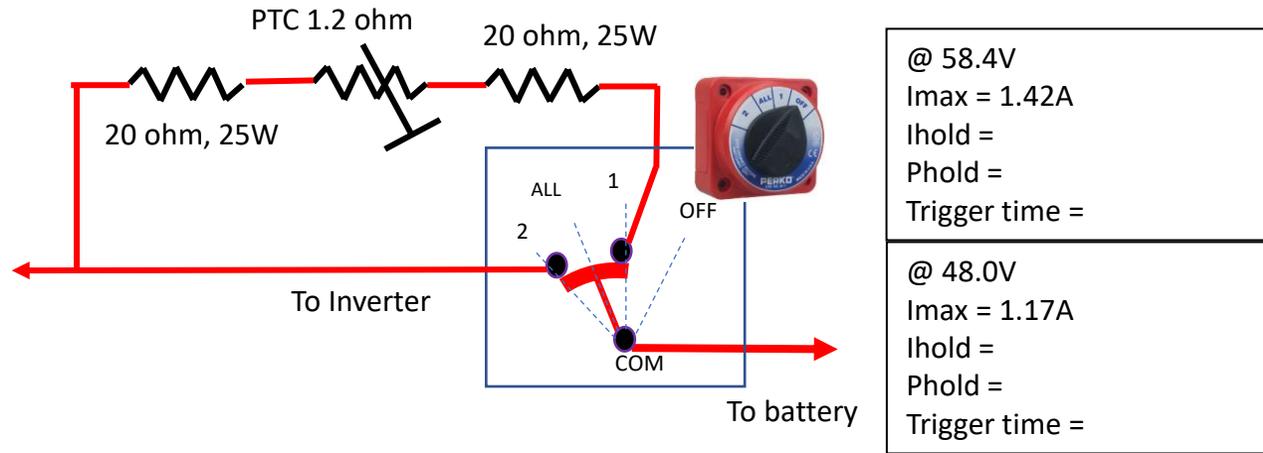**(Warning: I have not built/tested this design)**



## PTC specs

| Bulk Part Number   | Max. voltage | *1 Resistance Value at +25 °C | *2 Max. Current | *3 Hold Current |       | *4 Trip current |        | Dimensions (mm) |      |     |
|--------------------|--------------|-------------------------------|-----------------|-----------------|-------|-----------------|--------|-----------------|------|-----|
| Taping Part Number |              |                               |                 | +105°C          | +85°C | -10°C           | -40°C  | D               | H    | d   |
| PTGLCSAS1R2K3B51B0 | D.C. 51V     | 1.2ohm±10%                    | 5.0A            | 315mA           | 449mA | 1168mA          | 1270mA | 11.5            | 16.5 | 0.6 |
| PTGLCSAS1R2K3B51A0 |              |                               |                 |                 |       |                 |        |                 |      |     |

## Operation:

### Turn ON

1. Ensure inverter is off
2. Turn switch to position '1' for ~2 second
3. Turn switch to position 'All' or '2'
4. Turn on inverter

### Turn Off

1. Turn off Inverter.
2. Turn Disconnect switch to 'Off' position.

Notice that this circuit requires a minimum of .185 amps during 'ptc hold' if the user leaves the inverter on and the switch in the '1' position. Otherwise the voltage on the PTC could exceed the spec of the device. The math works out that this should be OK, but I would feel a bit more comfortable with a higher max voltage spec on the PTC.

An alternative to the PTC is use a single 50W 40 ohm resistor in place of the ptc and two resistors. However, in this case, you might need to mount the resistor on a heat sync external to the switch in order to dissipate the heat during a miss-use condition.

# Assembly


Two 25W resistors  
Stacked and glued

Post 1

Common

PTC resistor  
soldered between  
resistors

Post 2

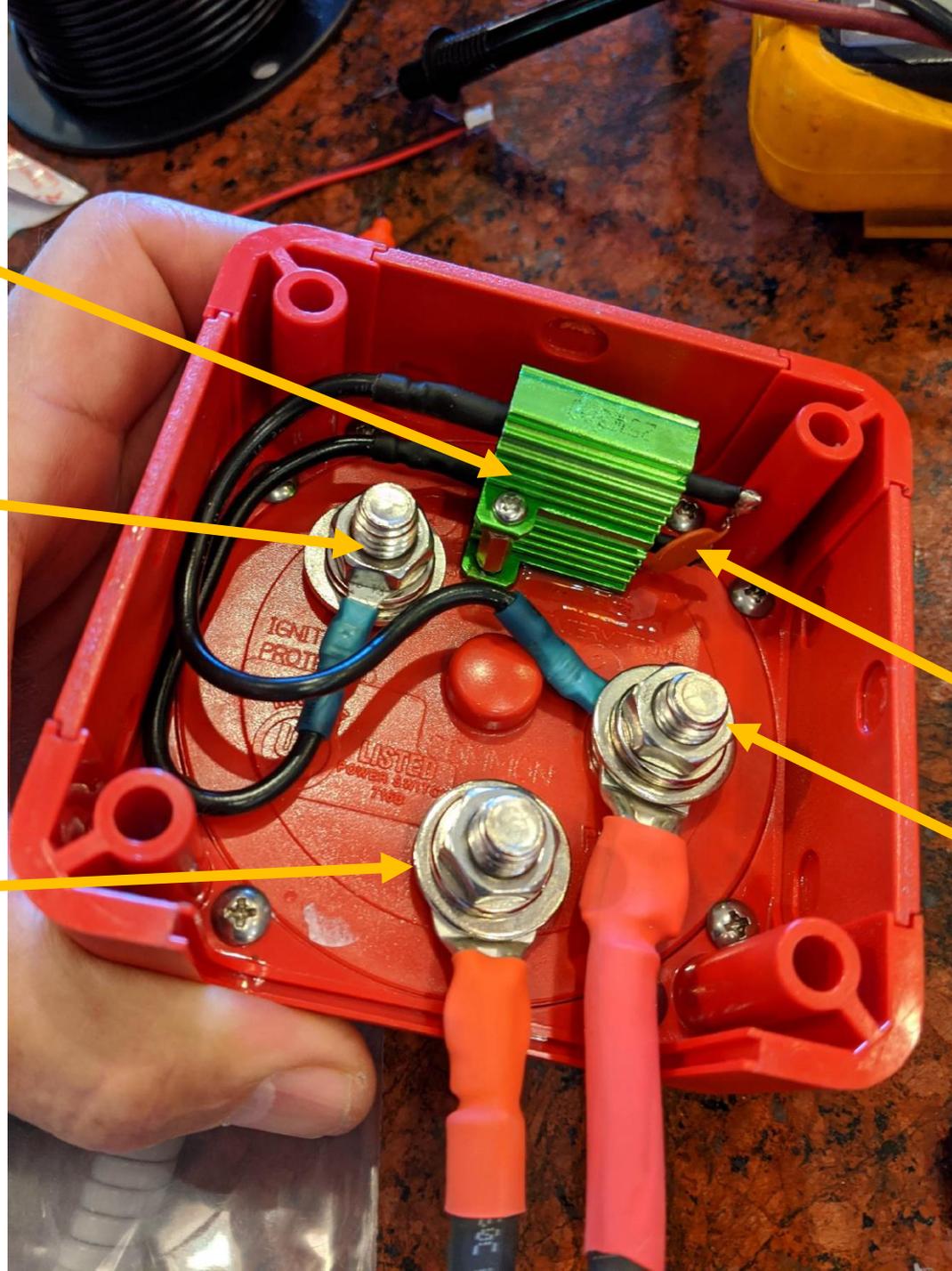

Label to help instruct the user



# Parts

## **Perko Switch:**

<https://www.ebay.com/p/1122213842>

Or

<https://www.ebay.com/itm/Perko-8511DP-Compact-Battery-Switch-7411/362536682888>

## **PTC Resistor: 1.2ohm, 5 Amp.**

[https://www.mouser.com/ProductDetail/Murata-Electronics/PTGLCSAS1R2K3B51B0?q\\_s=%2Fha2pyFadujTRLKUrNbfYMT8Oi18lPe7Yz7BN1JQeEARp4Zwl8415G5DFLgXHwgW/](https://www.mouser.com/ProductDetail/Murata-Electronics/PTGLCSAS1R2K3B51B0?q_s=%2Fha2pyFadujTRLKUrNbfYMT8Oi18lPe7Yz7BN1JQeEARp4Zwl8415G5DFLgXHwgW/)

## **3 ohm 25W resistor (12 V System)**

<https://www.ebay.com/itm/25W-3ohm-Wirewound-Power-Resistor-Aluminum-Hosing-Chassis-Mount/401838767539>

## **7 ohm 25W resistor (24 V System)**

<https://www.ebay.com/itm/US-Stock-2x-7-ohm-7R-25W-Watt-Aluminum-Housed-Metal-Case-Wirewound-Resistors/401396173511>